



تجزیه و تحلیل حلقه و کات است

امیر عباس شایگانی اکمل


تعریف درخت




- T یک درخت از گراف متصل به هم g گفته می شود چنانچه:
- T یک زیر گراف متصل به هم باشد.
 - T شامل تمام گره های g باشد.
 - T شامل هیچ حلقه ای نباشد.

شاخه های T را شاخه درخت و شاخه هایی از g را که در T نباشند، لینک می نامند.


مثالی از یک گراف و چند درخت آن

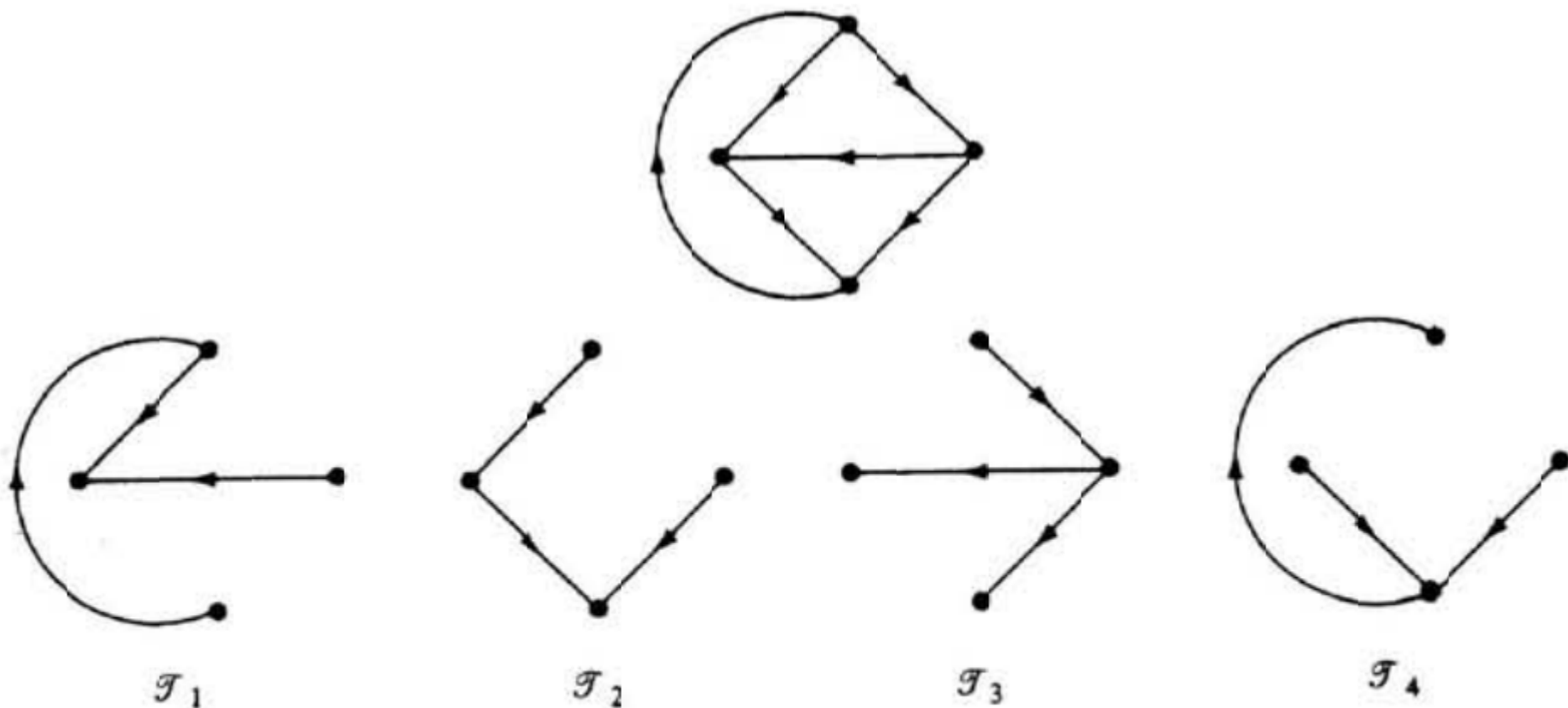


مثالی دیگر

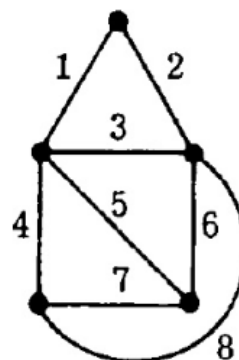


(الف) گراف g

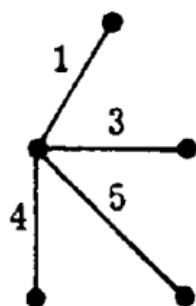


(ه) درخت T_4

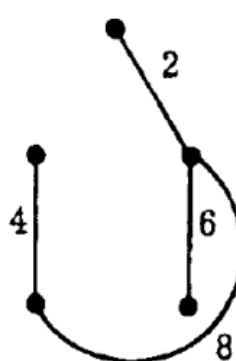

(د) درخت T_3

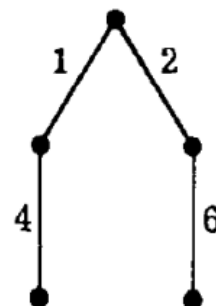

(ج) درخت T_2

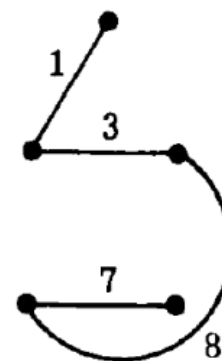

(ب) درخت T_1



قضیه اساسی نظریه گراف

گراف متصل به هم g با n_t گره و b شاخه و یک درخت T از g داده شده‌اند


۱- میان هر جفت گره از g مسیر یکتایی در روی درخت وجود دارد.

۲- $n_t - 1$ شاخه درخت و $b - n_t + 1$ لینک وجود دارند.

۳- هر لینک T و مسیر یکتای میان گره‌های دوسر آن در روی درخت، حلقه یکتایی تشکیل می‌دهد
(این حلقه را حلقه اساسی متناظر با لینک گویند).

۴- هر شاخه درخت T همراه با بعضی از لینک‌ها، کاتست یکتایی از g را تعریف می‌کند. این کاتست را کاتست اساسی متناظر با آن شاخه درخت گویند. به عبارت دیگر به تعداد شاخه‌های درخت کاتست اساسی داریم.

مثال قضیه اساسی نظریه گراف

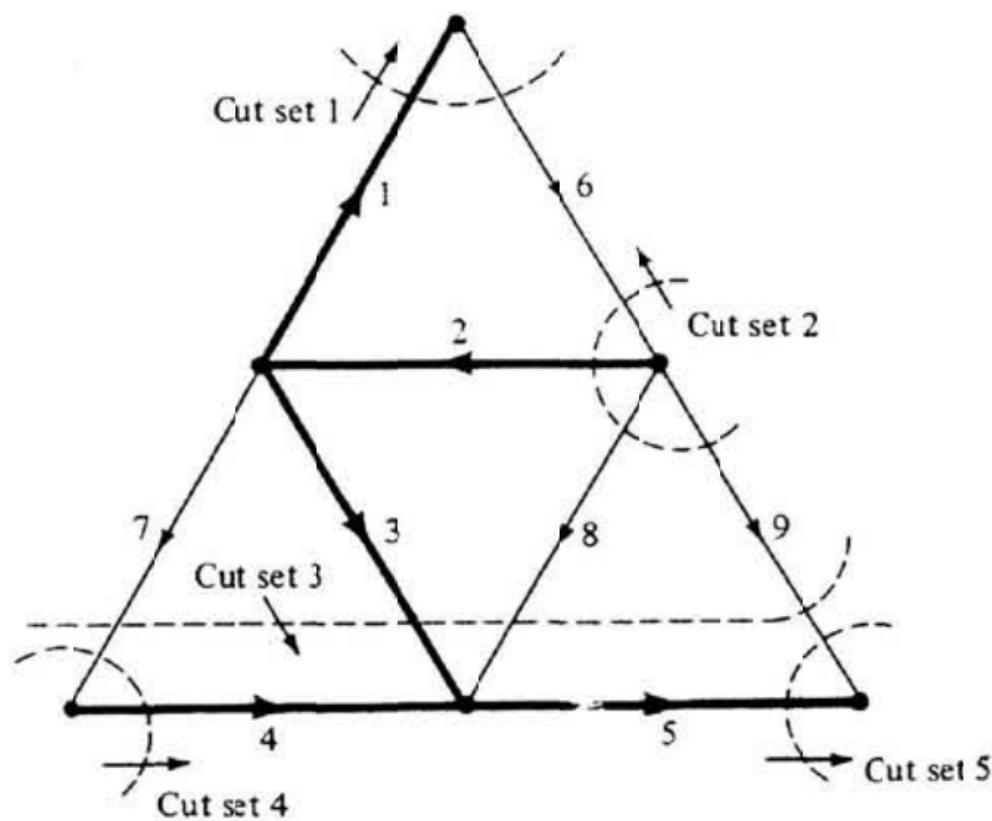

set 1:

$$i_1 - i_6 = 0$$

set 2:

$$i_2 - i_6 + i_8 + i_9 = 0$$

set 3:

$$i_3 + i_7 + i_8 + i_9 = 0$$

set 4:

$$i_4 - i_7 = 0$$

set 5:

$$i_5 + i_9 = 0$$



Cut set 1: $i_1 - i_6 = 0$

Cut set 2: $i_2 - i_6 + i_8 + i_9 = 0$

Cut set 3: $i_3 + i_7 + i_8 + i_9 = 0$

Cut set 4: $i_4 - i_7 = 0$

Cut set 5: $i_5 + i_9 = 0$

$$Q = [1_{n-1}, Q_\ell]$$

$$n-1 \text{ Cut sets} \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & -1 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \end{bmatrix} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ \cdot \\ \cdot \\ i_9 \end{bmatrix}}_{\ell \text{ links}} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$


$\underbrace{\hspace{10em}}_{n-1 \text{ twigs} \hspace{10em}}$

$$Q_i = 0 \quad (3.2)$$

where Q is an $(n - 1) \times b$ matrix called the *fundamental cut-set matrix* associated with a tree \mathcal{T} . Its jk th element is defined as follows:

$$q_{jk} = \begin{cases} 1 & \text{if branch } k \text{ belongs to cut set } j \\ & \text{and has the same direction} \\ -1 & \text{if branch } k \text{ belongs to cut set } j \\ & \text{and has the opposite direction} \\ 0 & \text{if branch } k \text{ does not belong to} \\ & \text{cut set } j \end{cases}$$

معادلات KVL

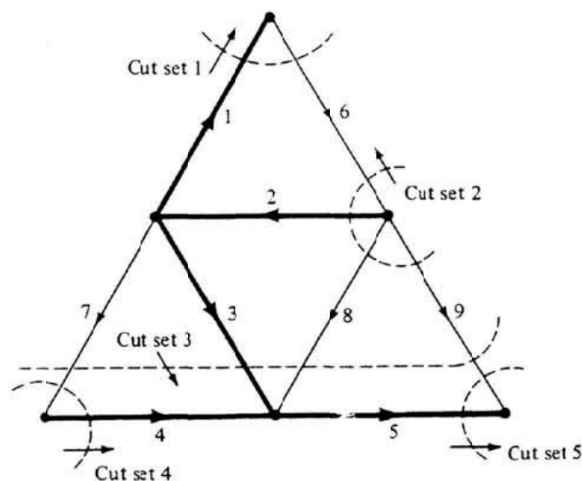

$$\mathbf{v} = \mathbf{Q}^T \mathbf{v}_t$$

$$v_1 = v_{t1}$$

$$v_2 = v_{t2}$$

$$v_3 = v_{t3}$$

$$v_4 = v_{t4}$$

$$v_5 = v_{t5}$$

$$v_6 = -v_1 - v_2 = -v_{t1} - v_{t2}$$

$$v_7 = v_3 - v_4 = v_{t3} - v_{t4}$$

$$v_8 = v_2 + v_3 = v_{t2} + v_{t3}$$

$$v_9 = v_2 + v_3 + v_5 = v_{t2} + v_{t3} + v_{t5}$$

$$\begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ \vdots \\ \vdots \\ v_9 \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \\ -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 1 \end{bmatrix}}_{n-1} \begin{bmatrix} v_{t1} \\ v_{t2} \\ v_{t3} \\ v_{t4} \\ v_{t5} \end{bmatrix}$$



جمع بندی نتایج تعریف درخت

Kirchhoff's equations based on the fundamental cut-set matrix \mathbf{Q} of $(n - 1)$ rows and b columns:

$$\begin{aligned} \text{KCL:} \quad & \mathbf{Q}\mathbf{i} = \mathbf{0} \\ \text{KVL:} \quad & \mathbf{v} = \mathbf{Q}^T \mathbf{v}_t \end{aligned} \tag{3.6}$$

If twigs are labeled first from 1 to $n - 1$, then

$$\mathbf{Q} = [\mathbf{1}_{n-1}, \mathbf{Q}_\ell]$$

REMARKS

1. The two equations in (3.6) are generalizations of the following familiar Kirchhoff's equations based on nodes and the reduced incidence matrix \mathbf{A} :

KCL: $\mathbf{A}\mathbf{i} = \mathbf{0}$ (3.7)

KVL: $\mathbf{v} = \mathbf{A}^T \mathbf{e}$


2. Obviously, the fundamental cut-set matrix \mathbf{Q} associated with a tree represents a special case of the reduced cut-set matrix \mathbf{Q}_R introduced in Sec. 2. While for many digraphs, the reduced incidence matrix \mathbf{A} is a special case of the fundamental cut-set matrix, i.e., a tree can be chosen such that the \mathbf{Q} obtained is identical with the reduced incidence matrix for a particular datum node. This is not always possible as in the graph in Fig. 3.3.





نوشتن معادلات کات ست بصورت میانبر

- ۱- متغیرهای معادلات کات ست، ولتاژ شاخه های درخت هستند.
- ۲- عناصر قطر اصلی برابر با مجموع ادمیتانسهای حاضر در کات ست مربوطه
- ۳- عناصر قطر فرعی A و Z لینکهای مشترک بین کات ست A و کات ست Z هستند. اگر جهت کات ست ها برای لینک مشترک مخالف باشد، علامت ادمیتانس آن منفی و در غیر این صورت علامت آن مثبت خواهد بود.
- ۴- جهت منبع جریان با جهت مخالف کات ست، مثبت و در غیر این صورت منفی خواهد بود.



مثال کات ست حالت دائم سینوسی

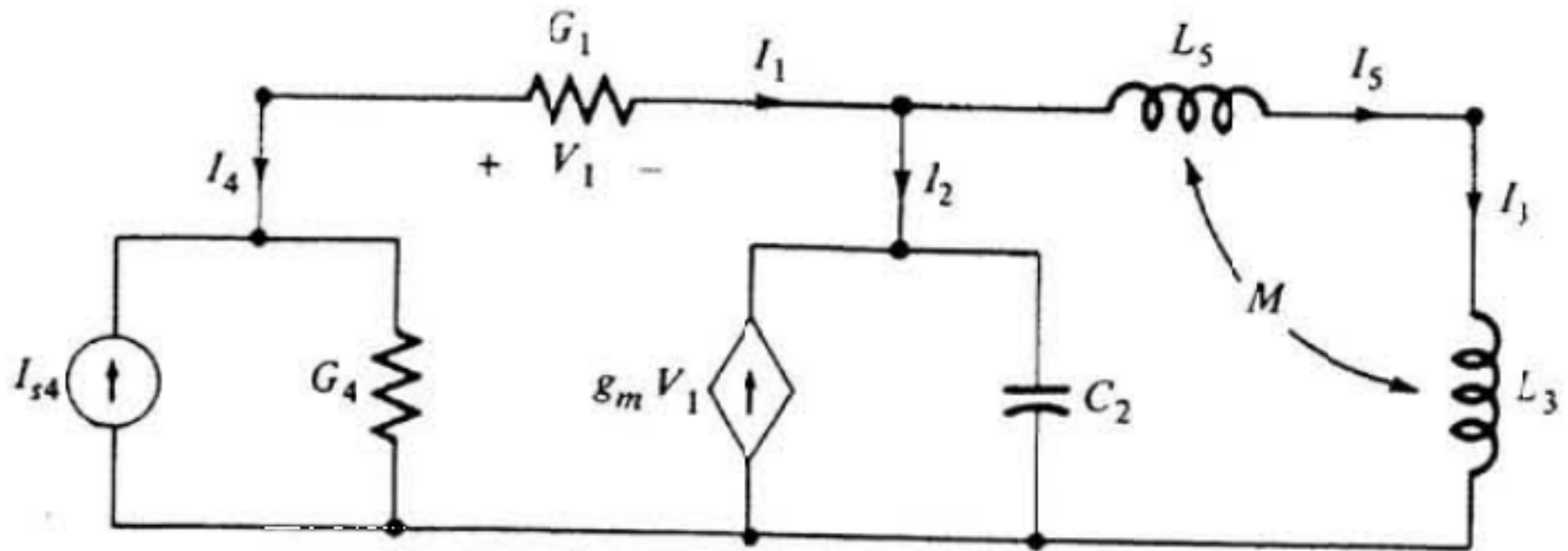

مثال کات ست، گراف و درخت

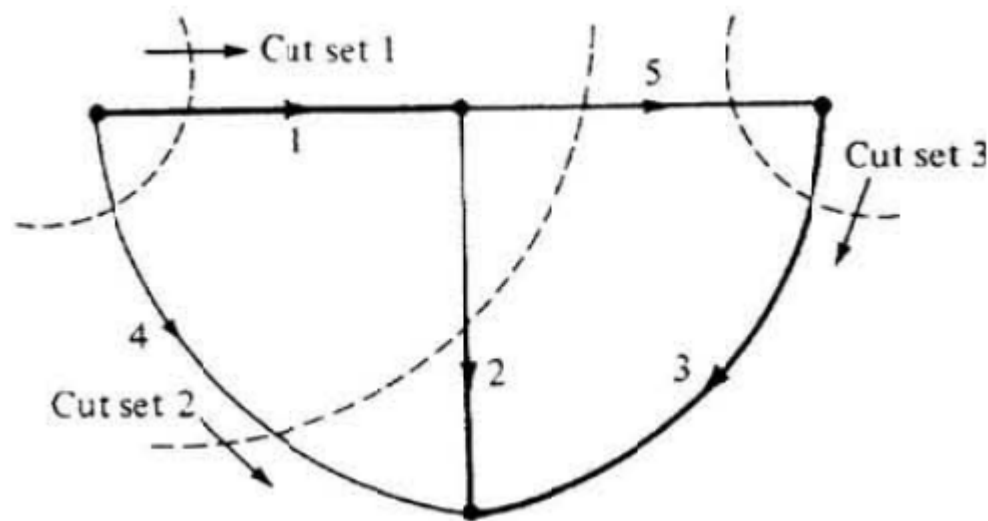
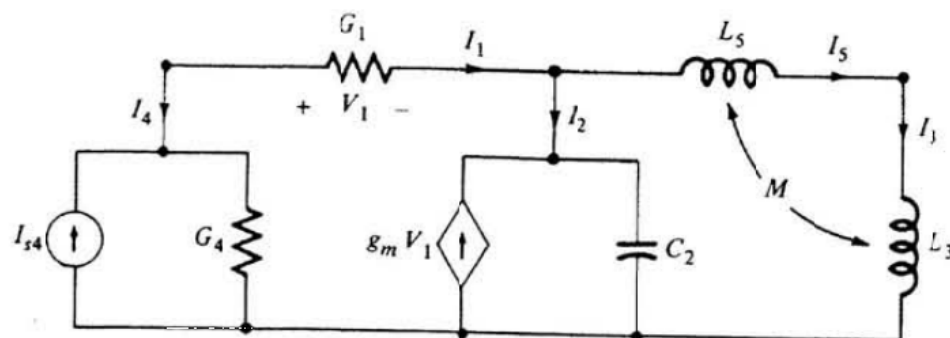


حل مثال کات ست

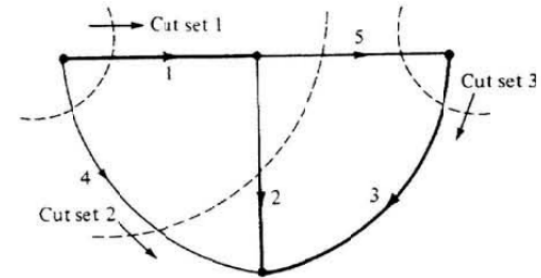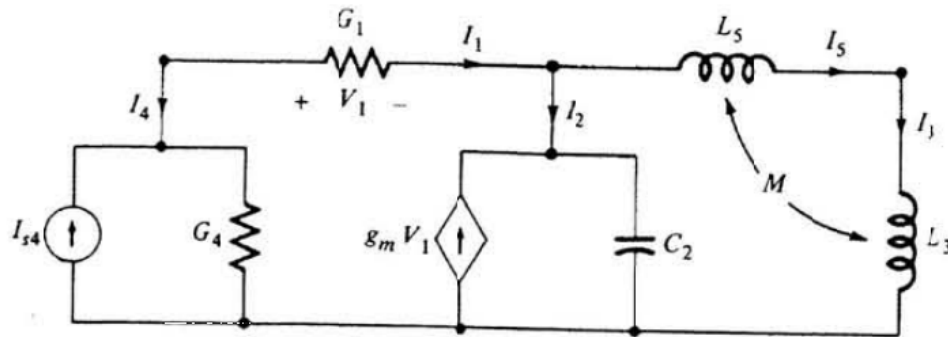

$$\begin{bmatrix} G_1 + G_4 & G_4 & 0 \\ G_4 & G_4 + \frac{1}{j\omega} \Gamma_5 + j\omega C_2 & -\frac{\Gamma_5}{j\omega} \\ 0 & -\frac{\Gamma_5}{j\omega} & \frac{1}{j\omega} (\Gamma_3 + \Gamma_5) \end{bmatrix}$$

حل مثال کات ست

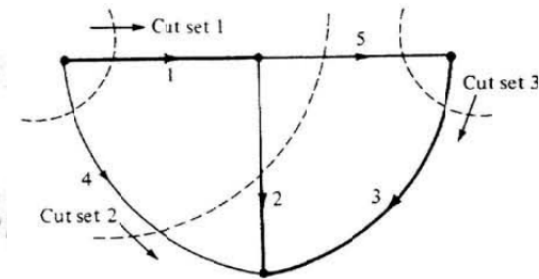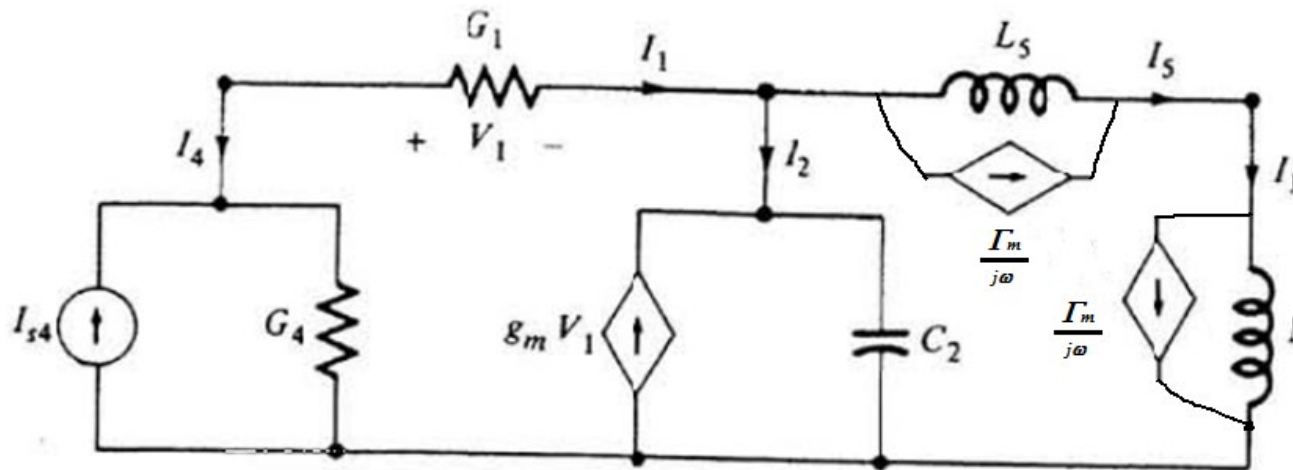


$$\begin{bmatrix} I_{s4} \\ I_{s4} + g_m V_1 - \frac{I_m}{j\omega} V_{t3} \\ \frac{I_m}{j\omega} V_{t3} - \frac{I_m}{j\omega} (V_{t2} - V_{t3}) \end{bmatrix}$$

حل مثال کات ست

$$\begin{bmatrix} G_1 + G_4 & G_4 & 0 \\ G_4 & G_4 + \frac{1}{j\omega} \Gamma_5 + j\omega C_2 & -\frac{\Gamma_5}{j\omega} \\ 0 & -\frac{\Gamma_5}{j\omega} & \frac{1}{j\omega} (\Gamma_3 + \Gamma_5) \end{bmatrix} \begin{bmatrix} I_{s4} \\ I_{s4} + g_m V_1 - \frac{\Gamma_m}{j\omega} V_B \\ \frac{\Gamma_m}{j\omega} V_B - \frac{\Gamma_m}{j\omega} (V_{t2} - V_{t3}) \end{bmatrix}$$

$$\begin{bmatrix} G_1 + G_4 & G_4 & 0 \\ G_4 - g_m & G_4 + \frac{1}{j\omega} \Gamma_5 + j\omega C_2 & -\frac{\Gamma_5}{j\omega} + \frac{\Gamma_m}{j\omega} \\ 0 & -\frac{\Gamma_5}{j\omega} + \frac{\Gamma_m}{j\omega} & \frac{1}{j\omega} (\Gamma_3 + \Gamma_5 + 2\Gamma_m) \end{bmatrix}$$

تجزیه و تحلیل حلقه

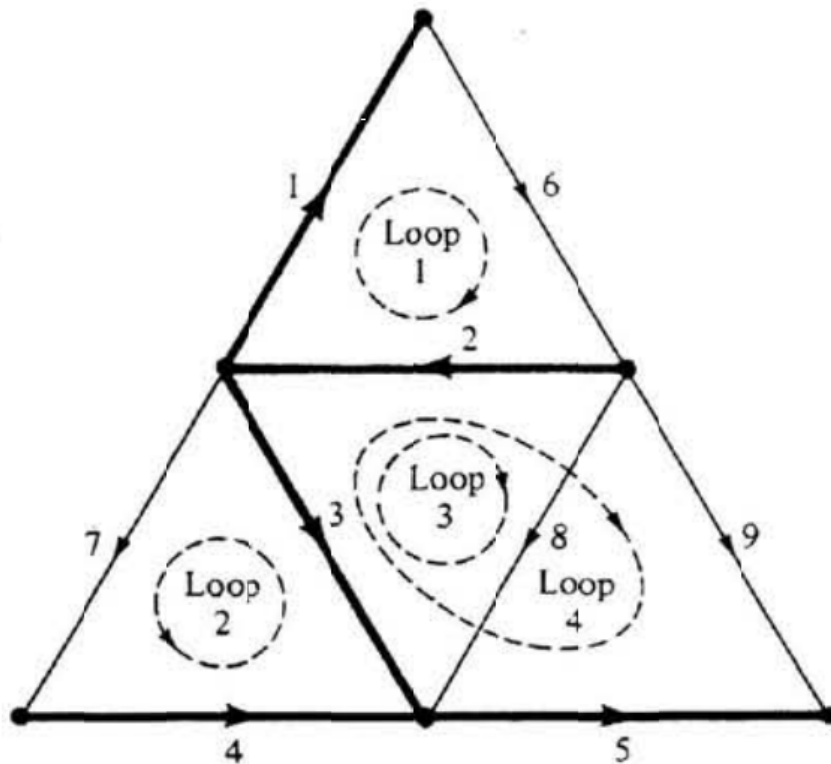

Loop 1:

$$v_6 + v_1 + v_2 = 0$$

Loop 2:

$$v_7 - v_3 + v_4 = 0$$

Loop 3:

$$v_8 - v_2 - v_3 = 0$$

Loop 4:

$$v_9 - v_2 - v_3 - v_5 = 0$$

نوشتن معادلات حلقه



Loop 1: $v_5 + v_1 + v_2 = 0$

Loop 2: $v_7 - v_3 + v_4 = 0$

Loop 3: $v_8 - v_2 - v_3 = 0$

Loop 4: $v_9 - v_2 - v_3 - v_5 = 0$

$$\ell \text{ loops} \begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ 0 & -1 & -1 & 0 & 0 \\ 0 & -1 & -1 & 0 & -1 \end{bmatrix} \underbrace{\hspace{10em}}_{n-1 \text{ twigs}} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \underbrace{\hspace{10em}}_{\ell \text{ links}} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ \vdots \\ \vdots \\ v_9 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \mathbf{Bv} = \mathbf{0}$$




$$\mathbf{B}\mathbf{v} = \mathbf{0}$$

$$\mathbf{B} = [\mathbf{B}_t, \mathbf{1}_t]$$

where \mathbf{B} is an $\ell \times b$ matrix called the *fundamental loop matrix* associated with the tree \mathcal{T} . Its jk th element is defined as follows:

$$b_{jk} = \begin{cases} 1 & \text{if branch } k \text{ is in loop } j \text{ and their} \\ & \text{reference directions are the same} \\ -1 & \text{if branch } k \text{ is in loop } j \text{ and their} \\ & \text{reference directions are opposite} \\ 0 & \text{if branch } k \text{ is not in loop } j \end{cases}$$

معادلات KCL

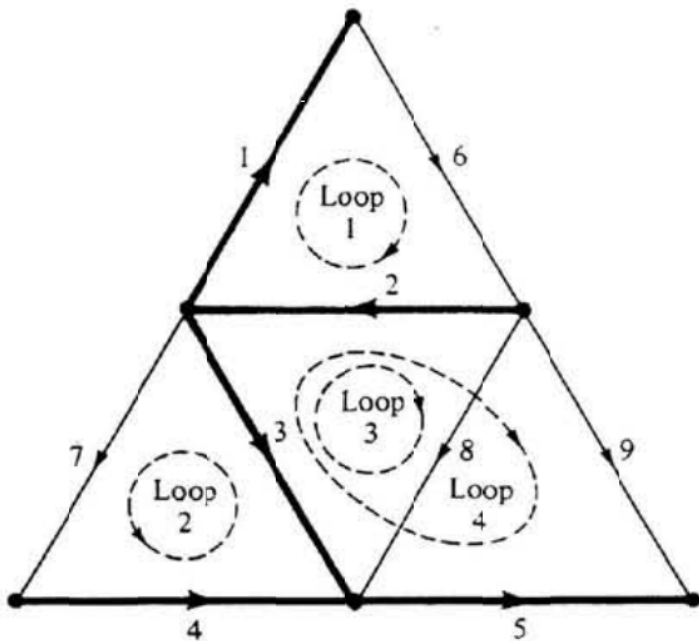

$$i_6 = i_{\ell 1}$$

$$i_7 = i_{\ell 2}$$

$$i_8 = i_{\ell 3}$$

$$i_9 = i_{\ell 4}$$

$$i_1 = i_{\ell 1}$$

$$i_2 = i_{\ell 1} - i_{\ell 3} - i_{\ell 4}$$

$$i_3 = -i_{\ell 2} - i_{\ell 3} - i_{\ell 4}$$

$$i_4 = i_{\ell 2}$$

$$i_5 = -i_{\ell 4}$$

نوشتن KCL



$$i_1 = i_{\ell 1}$$

$$i_2 = i_{\ell 1} - i_{\ell 3} - i_{\ell 4}$$

$$i_3 = -i_{\ell 2} - i_{\ell 3} - i_{\ell 4}$$

$$i_4 = i_{\ell 2}$$

$$i_5 = -i_{\ell 4}$$

$$i_6 = i_{\ell 1}$$

$$i_7 = i_{\ell 2}$$

$$i_8 = i_{\ell 3}$$

$$i_9 = i_{\ell 4}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_9 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 1 & 0 & -1 & -1 \\ 0 & -1 & -1 & -1 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{\ell 1} \\ i_{\ell 2} \\ i_{\ell 3} \\ i_{\ell 4} \end{bmatrix}$$

$\underbrace{\hspace{10em}}_{\ell}$

$$\mathbf{i} = \mathbf{B}^T \mathbf{i}_{\ell}$$

Kirchhoff's equations based on the fundamental loop matrix \mathbf{B} of ℓ rows and b columns

$$\text{KVL:} \quad \mathbf{B}\mathbf{v} = \mathbf{0} \quad (3.13)$$

$$\text{KCL:} \quad \mathbf{i} = \mathbf{B}^T \mathbf{i}_\ell$$

If twigs are numbered first from 1 to $n - 1$,

$$\mathbf{B} = [\mathbf{B}_t, \mathbf{1}_\ell]$$

REMARKS

1. The fundamental loop matrix \mathbf{B} associated with a tree \mathcal{T} is obviously a special case of the reduced loop matrix \mathbf{B}_R . In deriving the KVL equations $\mathbf{B}\mathbf{v} = \mathbf{0}$ based on a tree, we have demonstrated that \mathbf{B} is of rank $\ell = b - (n - 1)$. Thus the number of a maximal and linearly independent set of KVL equations based on loops is equal to ℓ , i.e., \mathbf{B}_R is of rank ℓ .
2. We have mentioned duality in deriving the fundamental loop matrix \mathbf{B} from the fundamental cut-set matrix \mathbf{Q} . It should be clear to the reader by now that there indeed exist many dual terms. We summarize some of these in Table 3.1.



نوشتن معادلات حلقه بصورت میانبر

۱- متغیرهای معادلات حلقه، جریان لینک‌های مربوط به درخت مورد نظر هستند.

۲- عناصر قطر اصلی برابر با مجموع امیدانسه‌های حاضر در حلقه

۳- عناصر قطر فرعی A و Z شاخه‌های مشترک بین حلقه A و حلقه Z هستند. اگر جهت حلقه‌ها برای شاخه مشترک یکسان باشد، علامت امیدانس آن مثبت و در غیر این صورت علامت آن منفی خواهد بود.

۴- برای علامت منبع ولتاژ اگر حلقه با قطب منفی منبع برخورد می‌کند، مثبت در نظر گرفته می‌شود و در غیر این صورت منفی خواهد بود.

Table 3.1 Dual terms in loop and cut-set analysis

Loop analysis	Cut-set analysis
Link	Twig
Fundamental loop	Fundamental cut set
Link current, i_l	Twig voltage, v_t
Fundamental loop matrix, B	Fundamental cut-set matrix, Q

رابطه بین Q و B



Theorem Let \mathbf{Q} and \mathbf{B} be the fundamental cut-set matrix and the fundamental loop matrix, respectively, of a connected digraph \mathcal{G} for a specified tree \mathcal{T} ; then

$$\mathbf{B}\mathbf{Q}^T = \mathbf{0} \quad (3.14)$$

PROOF We have, for an arbitrary twig voltage vector $\mathbf{v}_t = [v_{t1}, v_{t2}, \dots, v_{t(n-1)}]^T$,

$$\mathbf{v} = \mathbf{Q}^T \mathbf{v}_t \quad (3.15)$$

This says that the b -vector \mathbf{v} is expressed by KVL in terms of linear combinations of v_{tk} 's by the matrix \mathbf{Q}^T . Next, we have, by KVL, a set of linear constraints on the b -vector \mathbf{v} , given by

$$\mathbf{B}\mathbf{v} = \mathbf{0} \quad (3.16)$$

Thus, premultiplying Eq. (3.15) by \mathbf{B} and using Eq. (3.16), we obtain

$$\mathbf{B}\mathbf{Q}^T \mathbf{v}_t = \mathbf{0} \quad \text{for all } \mathbf{v}_t \quad (3.17)$$

Thus,

$$\mathbf{B}\mathbf{Q}^T = \mathbf{0}$$

رابطه بین زیر ماتریسهای Q و B



$$Q = [\mathbf{1}_{n-1}, \mathbf{Q}_\ell]$$

and

$$\mathbf{B} = [\mathbf{B}_\ell, \mathbf{1}_\ell]$$

$$\mathbf{B}\mathbf{Q}^T = [\mathbf{B}_\ell, \mathbf{1}_\ell] \begin{bmatrix} \mathbf{1}_{n-1} \\ \mathbf{Q}_\ell^T \end{bmatrix}$$

$$= \mathbf{B}_\ell + \mathbf{Q}_\ell^T = \mathbf{0}$$

We obtain the identities

$$\mathbf{B}_\ell = -\mathbf{Q}_\ell^T \quad \text{and} \quad \mathbf{B}_\ell^T = -\mathbf{Q}_\ell$$