

$$i_{1\text{sr}} = V_c = V_1 \Rightarrow V_{1\text{sr}} = I_{1\text{sr}} \times 1 = V_c$$

$$\text{Law of Se: } V_1 + i_1 = C_1 \frac{dV_1}{dt} + i_{1\text{sr}} + i_{1\text{sr}} = \frac{i_{1\text{sr}} = V_1}{C_1} \quad i_1 = \frac{dV_1}{dt} + V_1 + i_{1\text{sr}}$$

$$\text{LVL ①} \Rightarrow i_1 + \frac{di_1}{dt} + V_1 = V_1$$


$$\text{LVL ②} \Rightarrow i_2 + \frac{di_2}{dt} = V_1$$

$$\frac{dV_1}{dt} = i_1 - V_1 - i_2$$

$$\frac{dV_1}{dt} = -V_1 - i_1 + V_s$$

$$\frac{di_2}{dt} = V_1 - \frac{i_2}{2}$$
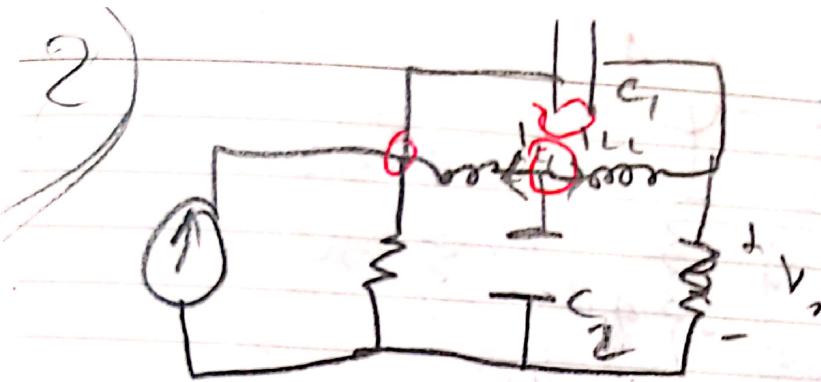
$$\begin{bmatrix} \frac{dV_1}{dt} \\ \frac{di_1}{dt} \\ \frac{di_2}{dt} \end{bmatrix} = \begin{bmatrix} -1 & 1 & -1 \\ -1 & -1 & 0 \\ 1 & 0 & -\frac{1}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ i_1 \\ i_2 \end{bmatrix} + \begin{bmatrix} 0 \\ V_s \\ 0 \end{bmatrix}$$



معادلہ کروں

$$KCL: i_{L1} + i_{L2} - 2 \frac{dV_{c1}}{dt} = 0 \Rightarrow \frac{dV_{c2}}{dt} = 2(i_{L1} + i_{L2})$$

$$KCL: i_{L1} + \frac{2V_{c1}}{R_L} + i_s = -\frac{V_{c2} - 2 \frac{dV_{c1}}{dt}}{R_L} = 0$$

$$KVL: -V_{c2} + 3 \frac{dV_{c2}}{dt} + i_{L2} - 2 \frac{dV_{c1}}{dt} = 0$$


$$KVL: 2di_{L1} - 3 \frac{di_{L2}}{dt} + V_{c1} = 0 \Rightarrow V_{1c} - V_{2c} + \frac{2di_{L1}}{R_L} + i_{L2} - \frac{2dV_{c1}}{R_L} = 0$$

$$\Rightarrow i_{L1} + i_{L2} + i_s - \frac{3}{2}V_{c2} + \frac{3di_{L1}}{R_L} + V_{c1} = 0$$

$$\frac{V_{c1}}{3} + V_{c2} - \frac{2(i_{L1} + i_{L2} + i_s)}{3} = \frac{3di_{L2}}{R_L}$$

$$\frac{dV_{c1}}{dt} = \frac{V_{c2}}{3} - \frac{2(i_s + i_{L2})}{3}$$

$$\begin{bmatrix} V_1 \\ V_2 \\ i_s \\ i_{L1} \\ i_{L2} \end{bmatrix} = \begin{bmatrix} 0 & 0 & 2 & 2 \\ 0 & \frac{2}{3} & -\frac{2}{3} & \frac{1}{6} \\ 0 & \frac{1}{3} & -\frac{1}{3} & -\frac{1}{3} \\ \frac{1}{2} & -\frac{1}{3} & -\frac{1}{3} & -\frac{1}{3} \\ \frac{1}{3} & \frac{1}{9} & -\frac{2}{9} & -\frac{2}{9} \end{bmatrix} + \begin{bmatrix} 0 \\ -\frac{1}{3}i_s \\ -\frac{1}{3}i_s \\ -\frac{1}{3}i_s \\ -\frac{2}{3}i_s \end{bmatrix}$$

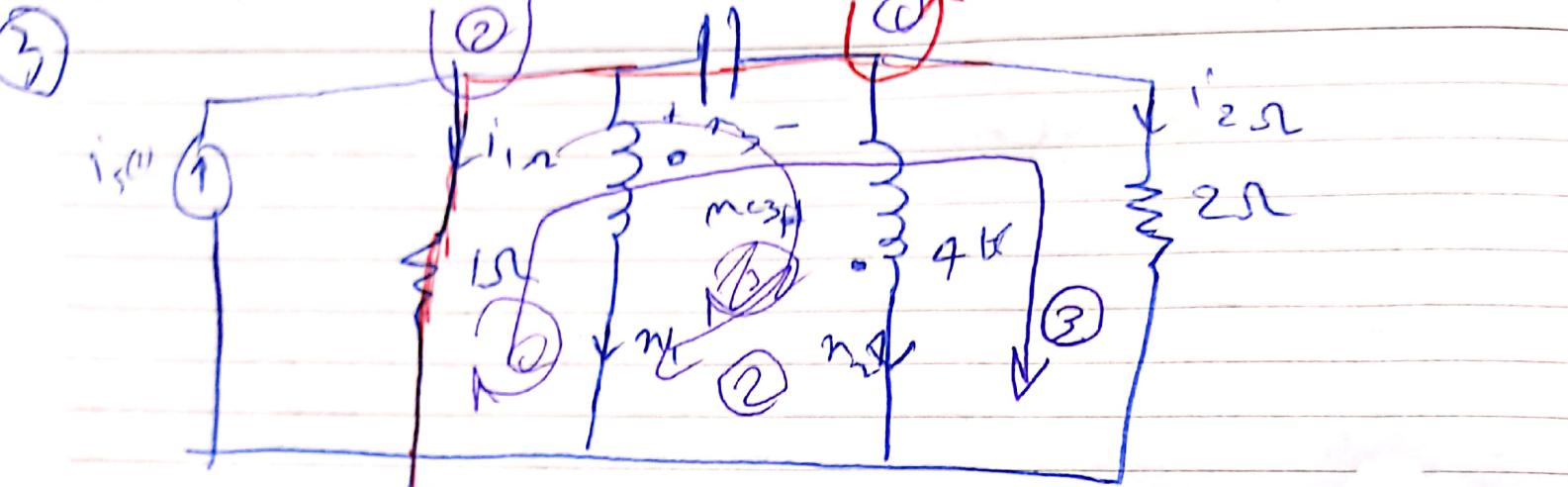

$$KCL: \frac{dn_3}{dt} = i_{1n} - i_{2n} + i_{2n} \quad (1)$$

$$KVL(1): 3 \frac{dx_1}{dt} - 3 \frac{dx_2}{dt} = 8V_{1n}$$

~~at Vce = 0~~

$$KVL(2): n_3 + 4 \frac{dx_2}{dt} - 3 \frac{dx_1}{dt} =$$

$$KVL(3): i_{1n} = x_3 + 2 \quad (2) \quad 2i_{2n} = i_{1n} - n_3 \quad (3)$$

$$KCL(2): i_{1n} = i_s - n_1 - n_2 - i_{2n}$$


(1) \rightarrow

$$\frac{dn_3}{dt} = 2n_2 + \frac{i_s}{3} - \frac{n_1}{3} - \frac{n_3}{3}$$


$$i_{2n} = \frac{i_s - n_1 - n_2 - n_3}{3}$$

$$\frac{di_1(0)}{dt} = ?$$

4)

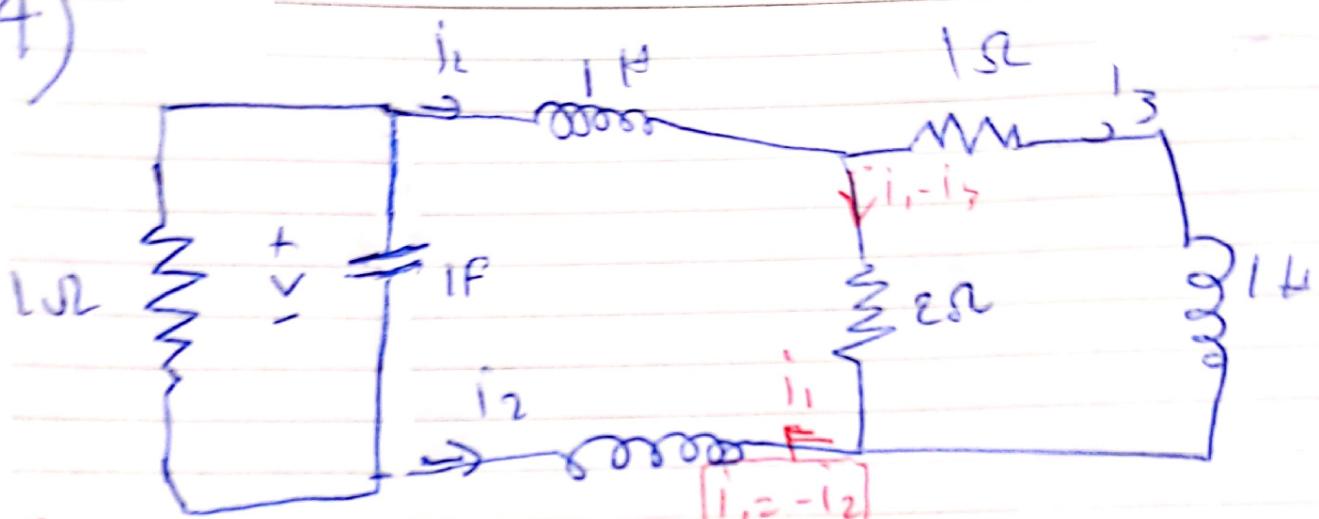

سلسلة مترادفة، مقدارها $i_1 = -i_2$

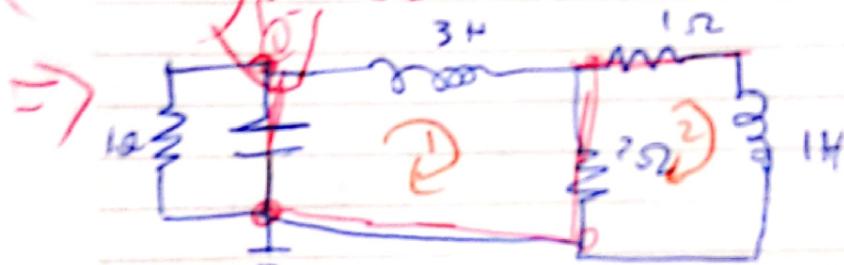

$$KCL \textcircled{1}: \frac{dV_c}{dt} = V_c - i_1$$

$$KVL \textcircled{1}: 3 \frac{di}{dt} = -2(i_1 - i_3) + V_c$$

$$KVL \textcircled{2}: \frac{di_3}{dt} = 2(i_1 - i_3) - i_3$$

$$\begin{bmatrix} \frac{dV_c}{dt} \\ \frac{di_1}{dt} \\ \frac{di_3}{dt} \end{bmatrix} = \begin{bmatrix} -1 & -1 & 0 \\ \frac{1}{3} & -\frac{2}{3} & \frac{2}{3} \\ 0 & 2 & -3 \end{bmatrix} \begin{bmatrix} V_c \\ i_1 \\ i_3 \end{bmatrix}$$

$$\textcircled{3} \quad \frac{di_1(0)}{dt} = \frac{1}{3}V(0) - \frac{2}{3}i(0) + \frac{2}{3}i_3(0)$$

دی

۹

چهارشنبه

2015 ١٣٩٤

30

December
Wednesday

١٨ ربیع الاولی ١٤٣٧

$$i_{L_1} = F_1(\Phi_{L_1})$$


$$\frac{dV_{C_1}}{dt} = F_2(\Phi_{C_1})$$

$$\Phi_{L_2} = F_3(i_{L_2})$$

$$i_C = \frac{d\Phi_{C_1}}{dt}$$

شنبه	یکم	دو	سه	چهارم	پنجم	ششم
۱۰	۱۱	۱۲	۱۳	۱۴	۱۵	۱۶
۱۷	۱۸	۱۹	۲۰	۲۱	۲۲	۲۳
۲۴	۲۵	۲۶	۲۷	۲۸	۲۹	۳۰

5)

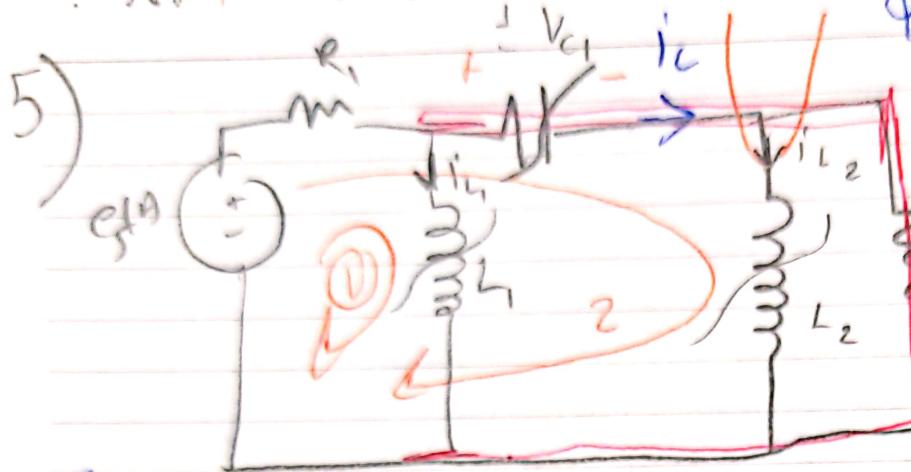

$$KCL \text{ ①: } i_C = i_{L_2} + \frac{d\Phi_{L_2}}{dt} \quad ①$$

$$KVL \text{ ②: } \frac{d\Phi_1}{dt} = e_s - R_1(i_C + i_{L_1}) = e_s - R_1 \left(i_{L_2} + \frac{d\Phi_{L_2}}{dt} + i_{L_1} \right) \quad ②$$

$$KVL \text{ ③: } V_{L_2} = \frac{d\Phi_2}{dt} = e_s - R_1 \left(i_{L_2} + \frac{1}{R_2} \frac{d\Phi_{L_2}}{dt} + i_{L_2} \right) - V_{C_1} \quad ③$$

$$\frac{d\Phi_1}{dt} = e_s(t) - R_1 \left(i_{L_1} + i_{L_2} + \frac{1}{R_2} \left(\frac{d\Phi_{L_1}}{dt} - V_{C_1} \right) \right)$$

$$\frac{d\Phi_1}{dt} = e_s(t) - R_1(i_{L_1} + i_{L_2} + \underbrace{\frac{1}{R_2} \frac{d\Phi_1}{dt}}_{\text{زیر}}) - \frac{V_{C_1}}{R_1}$$

$$(1 + \frac{R_1}{R_2}) \frac{d\Phi_1}{dt} = e_s(t) - R_1(F(\Phi_1)) - R_1 i_{L_2} + \frac{R_1}{R_2} F_2(\Phi_{C_1})$$

$$\frac{d\Phi_1}{dt} = \left(e_s(t) - R_1(F(\Phi_1)) - R_1 i_{L_2} + \frac{R_1}{R_2} F_2(\Phi_{C_1}) \right) \underbrace{\left(\frac{R_1}{R_1 + R_2} \right)}_{\text{زیر}}$$

5

$$\Rightarrow \frac{d\varphi_2}{dt} = \frac{[e_s(+) - R_1 F(\varphi_{c_1}) - R_1 i_{L_2} + \frac{R_1}{R_2} F_2(\varphi_{c_2})]}{(1 + \frac{R_1}{R_2}) F'_3(i_{L_2})} - \frac{F_2(\varphi_{c_2})}{F'_3(i_{L_2})}$$


⑤

③, ④

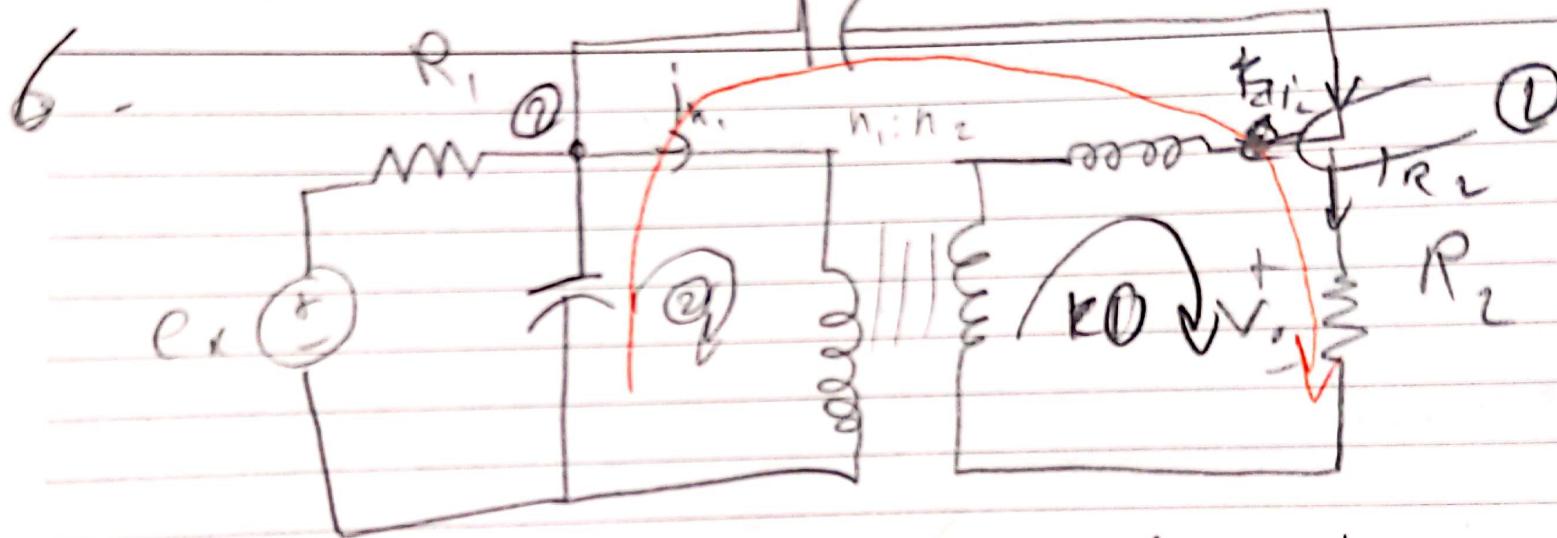1) $\frac{d\varphi_{c_1}}{dt}$

$$\frac{d\varphi_{c_1}}{dt} = i_{L_2} + \frac{[e_s(+) - R_1 F(\varphi_{c_1}) - R_1 i_{L_2} + \frac{R_1}{R_2} F_2(\varphi_{c_2})]}{(1 + \frac{R_1}{R_2}) \alpha R_2} - \frac{1}{R_2} f_2(\varphi_{c_2})$$

$$\Rightarrow \frac{d\varphi_{c_1}}{dt} = i_{L_2} + \frac{[e_s(+) - R_1 F(\varphi_{c_1}) - R_1 i_{L_2} + \frac{R_1}{R_2} F_2(\varphi_{c_2})]}{(R_2 + R_1)} - \frac{F_2(\varphi_{c_2})}{R_2}$$



KVL

$$\left. \begin{array}{l} \textcircled{1} \quad V_2 = \frac{n_2}{n_1} V_d \\ \textcircled{2} \quad V_2 + V_L = V_{R_2} \end{array} \right\} \quad \textcircled{1} \quad i_{C_2} = i_{R_2} + i_L \Rightarrow$$

\checkmark KVL: $V_{C_1} = V_{C_2} + V_{R_2} \Rightarrow V_{R_2} = -V_{C_1} + V_d \Rightarrow i_{R_2} = \frac{V_d - V_{C_2}}{R_2}$

\checkmark $\textcircled{2} \quad \frac{e_n(+) - V_{C_1}}{R_1} = i_{n_1} + i_{C_1} + i_{C_2} = i_{n_1} + i_{C_1} + i_L + i_{R_2}$

$$= C_1 V_1 + \frac{n_2}{n_1} i_L + \frac{V_{C_1} - V_{C_2}}{R_2} - i_L$$

$$\frac{n_2}{n_1} i_L + i_L = V_{C_1} - V_{C_2}$$

$$\begin{bmatrix} V_U \\ V_{C_1} \\ V_{C_2} \\ i_L \end{bmatrix} = \begin{bmatrix} \frac{G_1 + G_2}{C_1} & \frac{G_2}{C_1} & \frac{\left(1 - \frac{n_2}{n_1}\right)}{C_1} \\ C_1 & -G_2 & -1 \\ G_2 & -1 & 0 \\ \frac{1 - \frac{n_2}{n_1}}{L} & \frac{-1}{L} & 0 \end{bmatrix} \begin{bmatrix} V_{C_1} \\ V_{C_2} \\ i_L \end{bmatrix} + e_s(t) \begin{bmatrix} \frac{G_2}{C_1} \\ 0 \\ 0 \end{bmatrix}$$

$$V_o = V_{R_2} = V_{C_1} - V_{C_2} \Rightarrow V_o = [+1 \ -1 \ 0] \begin{bmatrix} V_{C_1} \\ V_{C_2} \\ i_L \end{bmatrix}$$