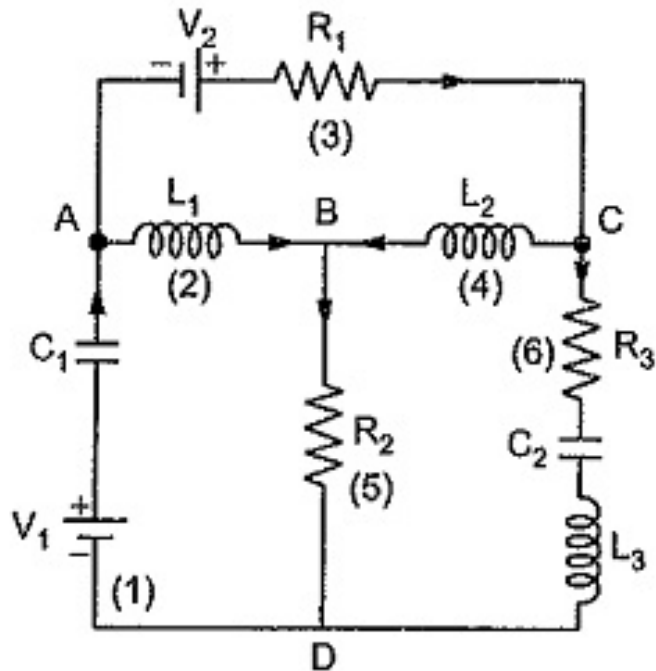





قضیه تلگان

امیر عباس شایگانی اکمل

یادآوری گراف



(a)

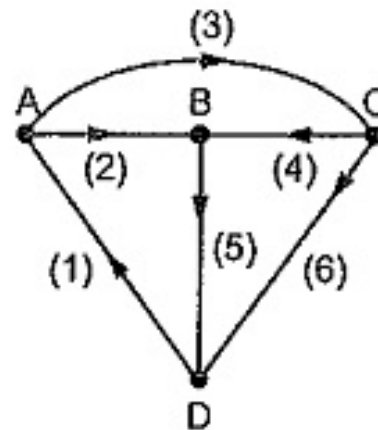


(b)

$$A_a = \begin{bmatrix} -1 & +1 & +1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & +1 & 0 \\ 0 & 0 & -1 & +1 & 0 & +1 \\ +1 & 0 & 0 & 0 & -1 & -1 \end{bmatrix}$$

$$A = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & +1 & 0 & +1 \end{bmatrix}$$

- برای تمام شبکه ها اعم از خطی، غیر خطی، متغیر با زمان یا نامتغیر با زمان قابل استفاده است. تفاوت نمی کند مقادیر اعداد، توابع یا فازورها استفاده شوند.

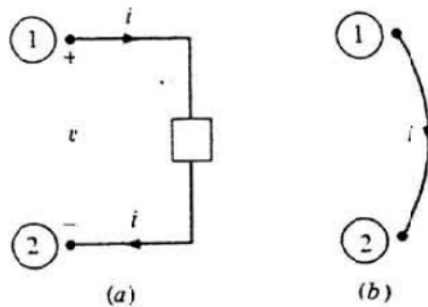- تنها محدودیت برای استفاده از قضیه تلگان، فشرده بودن مدار و صدق کردن قوانین **KVL** و **KCL** بر ولتاژها و جریان های شاخه ها است.



- رعایت جهت های قراردادی الزامی است.

بیان قضیه تلگان



Tellegen's theorem Consider an arbitrary circuit. Let the digraph \mathcal{G} have b branches. Let us use associated reference directions. Let $\mathbf{i} = (i_1, i_2, \dots, i_b)^T$ be *any* set of branch currents satisfying KCL for \mathcal{G} and let $\mathbf{v} = (v_1, v_2, \dots, v_b)^T$ be *any* set of branch voltages satisfying KVL for \mathcal{G} , then

$$\sum_{k=1}^b v_k i_k = 0 \quad \text{or equivalently} \quad \mathbf{v}^T \mathbf{i} = 0 \quad (7.1)$$

اثبات قضیه تلگان



$$\begin{aligned} V^T J &= (A^T e)^T J = (e^T (A^T)^T) J = (e^T A) J \\ &= e^T (AJ) = e(0) = 0 \end{aligned}$$



V بردار ولتاژ شاخه ها

J بردار جریان شاخه ها

e بردار ولتاژ گره ها



A ماتریس تلاقی گره با شاخه (مختصر شده)

مثال ۱

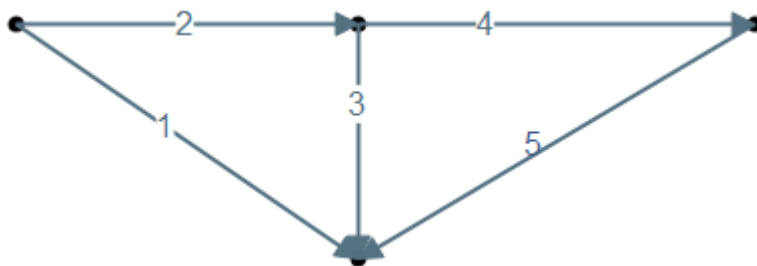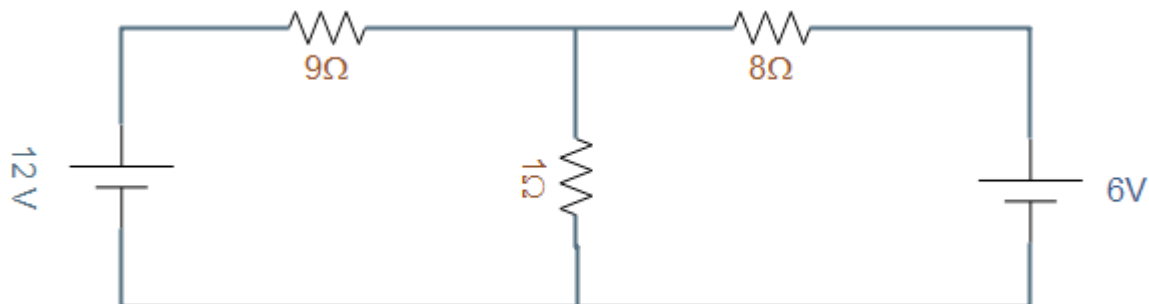

شاخه	۱	۲	۳	۴	۵
ولتاژ (ولت)	۱۲	۹	۳	-۳	۶
جریان (آمپر)	-۱	۱	۳	-۲	-۲
توان	-۱۲	۹	۹	۶	-۱۲

مثال ۲

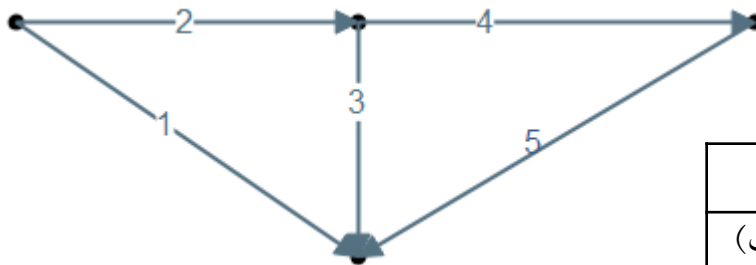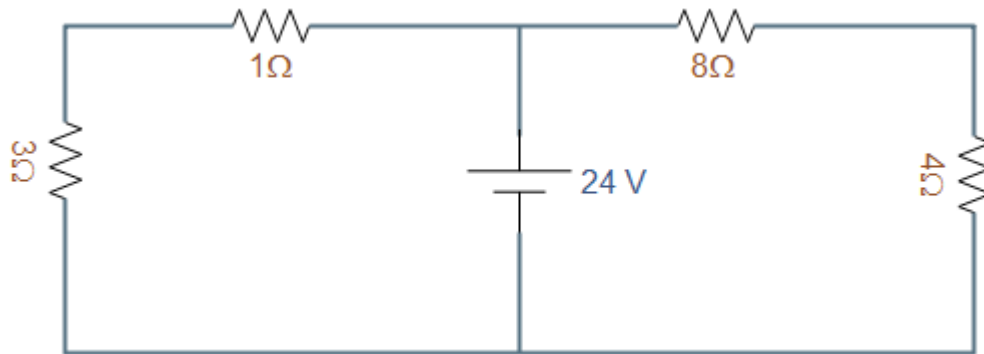

شاخه	۱	۲	۳	۴	۵
ولتاژ (ولت)	۱۸	-۶	۲۴	۱۶	۸
جریان (آمپر)	۶	-۶	-۸	۲	۲
توان	۱۰۸	۳۶	-۱۹۲	۳۲	۱۶

مثال ۳



شاخه	۱	۲	۳	۴	۵
ولتاژ (ولت) از مثال ۱	۱۲	۹	۳	-۳	۶
جریان (آمپر) از مثال ۲	۶	-۶	-۸	۲	۲
حاصلضرب ولتاژ در جریان شاخه	۷۲	-۵۴	-۲۴	-۶	۱۲

شاخه	۱	۲	۳	۴	۵
ولتاژ (ولت) از مثال ۲	۱۸	-۶	۲۴	۱۶	۸
جریان (آمپر) از مثال ۱	-۱	۱	۳	-۲	-۲
حاصلضرب ولتاژ در جریان شاخه	-۱۸	-۶	۷۲	-۳۲	-۱۶



مثال ۴



24 In the circuits shown in Fig. P1.24, let v_k and i_k be the branch voltage and current in circuit A and \hat{v}_k and \hat{i}_k be the branch voltage and current in circuit B. The following measurements have been obtained:

$$i_1 = 1 \text{ A} \quad \hat{v}_s = 3 \text{ V} \quad v_L = 2 \text{ V}$$

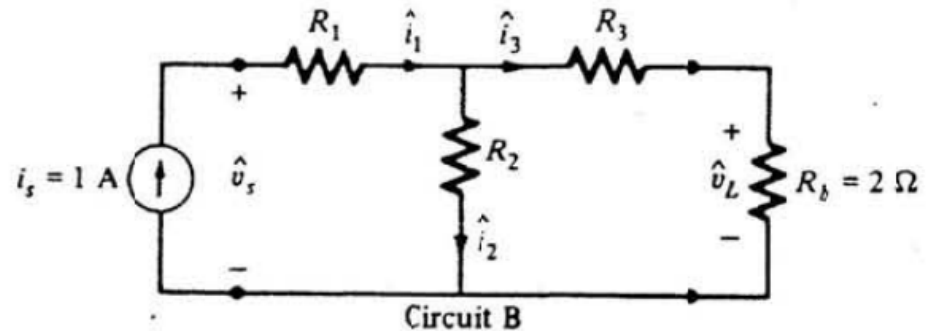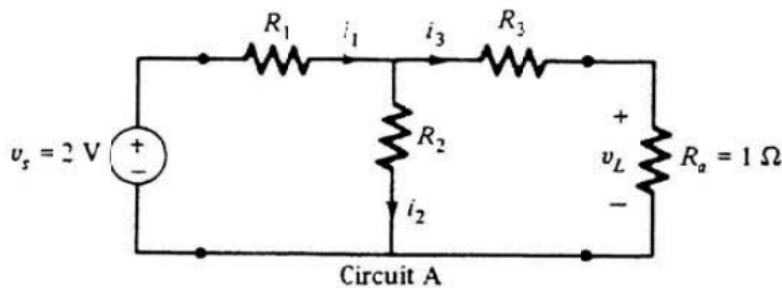Use a particular form of Tellegen's theorem to determine \hat{v}_L , where R_1 , R_2 , and R_3 are unknown resistors satisfying Ohm's law.





حل مثال ۴



$$\sum_{k=1}^5 v_k j_k = 0 \quad \sum_{k=1}^5 \widehat{v}_k \widehat{j}_k = 0$$
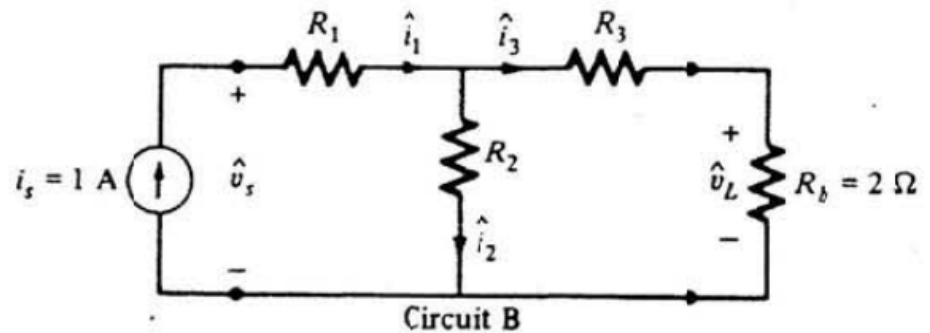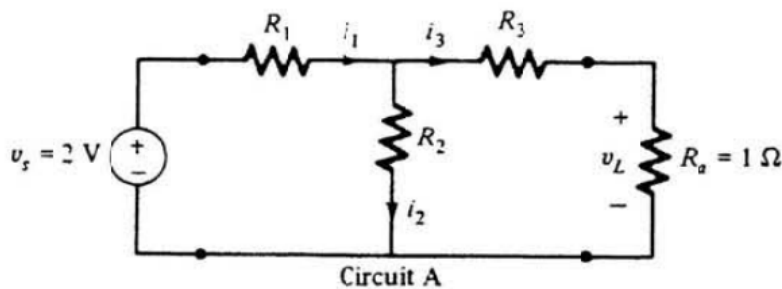
$$\sum_{k=1}^5 v_k \widehat{j}_k = 0 \quad \sum_{k=1}^5 \widehat{v}_k j_k = 0$$



$$\begin{aligned} & 2(-1) + R_1 i_1 \widehat{i}_1 + R_2 i_2 \widehat{i}_2 + R_3 i_3 \widehat{i}_3 + 2 \frac{\widehat{v}_L}{2} \\ & = 3(-1) + R_1 \widehat{i}_1 i_1 + R_2 \widehat{i}_2 i_2 + R_3 \widehat{i}_3 i_3 + \widehat{v}_L 2 \end{aligned}$$

$$\widehat{v}_L = 1$$

یکی از نتایج تلگان





20 Let N be a two-port made of arbitrary interconnections of linear two-terminal linear resistors (i.e., each resistor satisfies Ohm's law: $v_j = R_j i_j$). Consider the following two experiments:

Experiment 1. Drive N with two voltage sources v'_1 and v'_2 and measure the resulting port currents i'_1 and i'_2 , respectively. (See Fig. P1.20.)

Experiment 2. Drive N with two voltage sources v''_1 and v''_2 and measure the resulting port currents i''_1 and i''_2 , respectively.

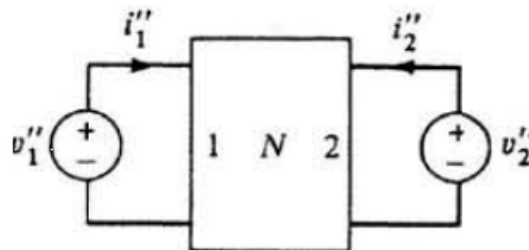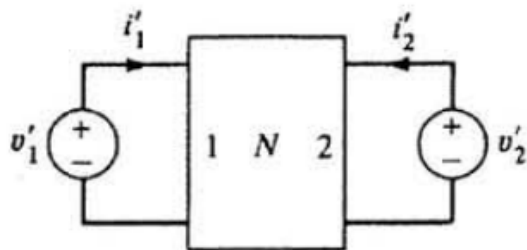
(a) Prove that the two sets of measurements are related as follows:

$$v'_1 i''_1 + v'_2 i''_2 = v''_1 i'_1 + v''_2 i'_2$$



این نتیجه برای حالت دائم سینوسی هنگامیکه شبکه N از RLC تشکیل شده باشد نیز معتبر است.
نکته: در حالت دائم سینوسی از فازورهای ولتاژ و جریان استفاده می شود.

امپدانس نقطه تحریک

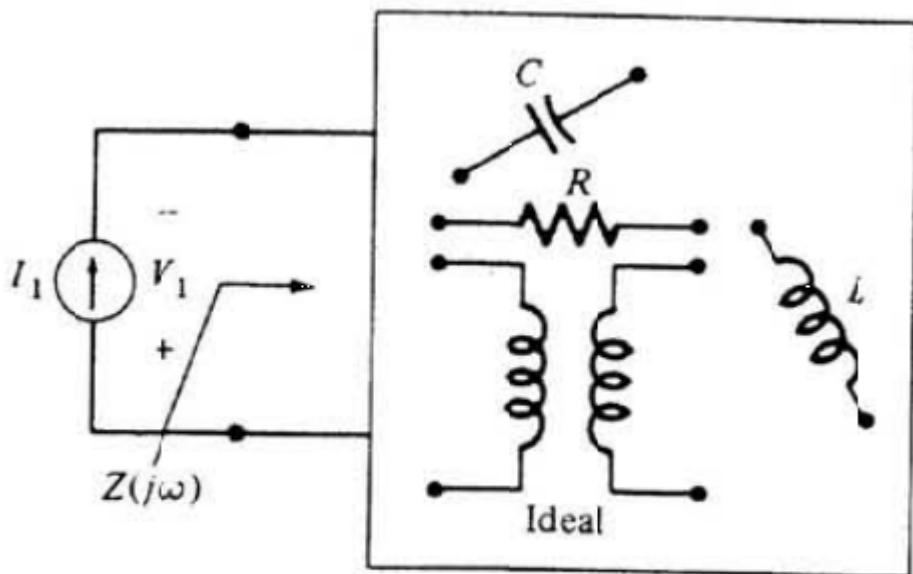

$$Z(j\omega) = \frac{2P_{\text{ave}} + 4j\omega[(\mathcal{E}_M(\omega) - \mathcal{E}_E(\omega))]}{|I_1|^2}$$

P_{ave} = average power dissipated in the resistors of \mathcal{N}

\mathcal{E}_M = average *magnetic* energy stored in \mathcal{N}

\mathcal{E}_E = average *electric* energy stored in \mathcal{N}



نتایج امیدانسی نقطه تحریک

COMMENTS

1. As expected $\text{Re}[Z(j\omega)]$ is $2P_{\text{ave}}/|I_1|^2$: The larger the dissipation, the larger the real part of the input impedance. [See also Eq. (5.15) above.]
2. If \mathcal{N} is purely *reactive* (only L 's and C 's, no resistors), then $Z(j\omega)$ is purely imaginary; furthermore $\text{Im}[Z(j\omega)] \triangleq X(j\omega)$ is positive or negative according to whether $\mathcal{E}_M(\omega) > \mathcal{E}_E(\omega)$ or vice versa. [Recall the series RL , $Z = R + j\omega L$, or the series RC circuit, $Z = R - j(1/\omega C)$.]
3. Equation (5.38) implies the following facts:

- (a) If \mathcal{N} consists only of *passive resistors* and/or *passive inductors*—often called a passive RL circuit—then

$$0 \leq \angle Z(j\omega) \leq 90^\circ \quad \text{for all real } \omega\text{'s}$$

- (b) If \mathcal{N} consists only of *passive resistors* and/or *passive capacitors*—called a passive RC circuit—then

$$-90^\circ \leq \angle Z(j\omega) \leq 0 \quad \text{for all real } \omega\text{'s}$$

- (c) In the general case, if \mathcal{N} has only *passive* R 's, L 's, C 's, transformers, and gyrators, then

$$-90^\circ \leq \angle Z(j\omega) \leq +90^\circ \quad \text{for all real } \omega\text{'s}$$

or equivalently

$$\text{Re}[Z(j\omega)] \geq 0 \quad \text{for all real } \omega\text{'s}$$

4. Similar conclusions hold for $Y(j\omega)$, by duality.