



قضیه تلگان (ادامه بحث)

امیر عباس شایگانی اکمل

قضیه هم پاسخی





21 Let N be the two-port described in Prob. 20. Consider the following experiments


Experiment 1. Drive port 1 with a voltage source with voltage E and measure the current i_2' in the short circuit across port 2. (See Fig. P1.21.)

Experiment 2. Drive port 2 with a voltage source with an identical voltage E and measure the current i_1'' in the short circuit across port 1.

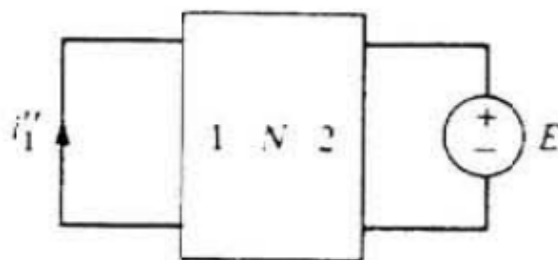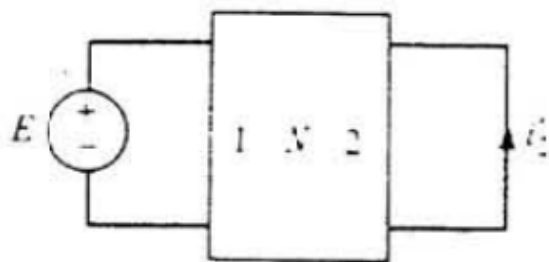Prove that $i_2' = i_1''$, and state this remarkable property in words (reciprocity property).



اثبات هم پاسخی

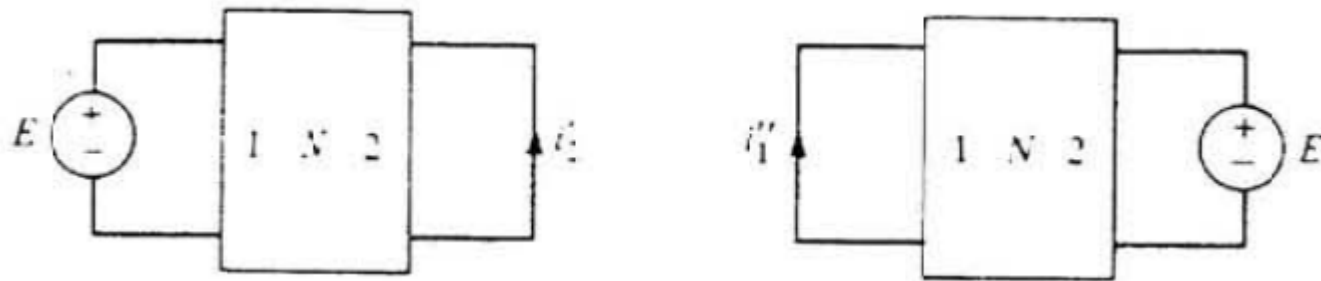

$$-E i_1'' + 0 = 0 - E i_2'$$

$$i_1'' = i_2'$$

مثال برای قضیه تلگان



25 Consider the circuit shown in Fig. P1.25. Two sets of measurements on this circuit give the following results:

(i) When $R_L = 2\ \Omega$: $v_1 = 8\ \text{V}$ $i_1 = -2\ \text{A}$ $v_L = 2\ \text{V}$

(ii) When $R_L = 4\ \Omega$: $\hat{v}_1 = 12\ \text{V}$ $\hat{i}_1 = -2.4\ \text{A}$ $\hat{v}_L = ?$

Determine \hat{v}_L , given that R_1 , R_2 , R_3 , and R_4 are linear resistors satisfying Ohm's law.

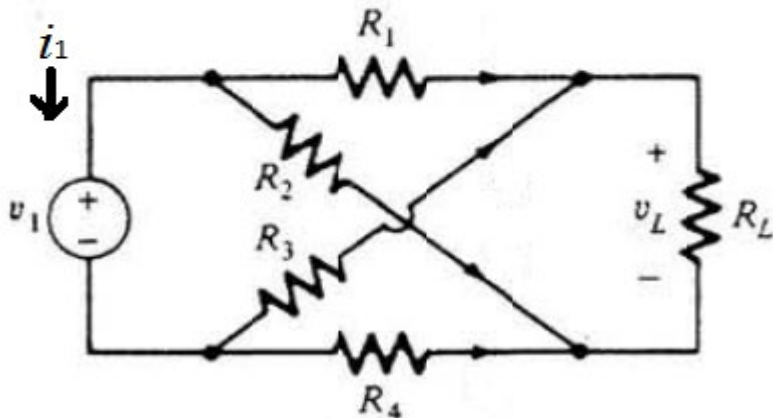


Figure P1.25

حل مثال



شاخه	منبع ۱	منبع ۲	بار ۱	بار ۲
ولتاژ (ولت)	۸	۱۲	۲	v_L
جریان (آمپر)	-۲	-۲/۴	۱	$v_L/4$

$$8 * (-2.4) + 2 * \frac{v_L}{4} = 12 * -2 + v_L$$

$$4.8 = v_L/2$$

$$9.6 = v_L$$



$$A_m \cos(\omega t + \phi) \quad (1.1)$$

where the *amplitude* A_m , the *phase* ϕ , and the *frequency* ω are real *constants*. The amplitude A_m is always taken to be *positive*. The frequency ω is measured in radians per second. The *period* is $T = 2\pi/\omega$ in seconds.

If the frequency is measured in hertz and labeled f , then the sinusoid becomes $A_m \cos(2\pi ft + \phi)$ and $T = 1/f$.

To the sinusoid above we associate a complex number A called the *phasor* (of that sinusoid) according to the rule

$$A \triangleq A_m e^{j\phi} \quad (1.2)$$

روابط شاخه ها



Resistor:	$v(t) = R i(t)$	$V = RI$	(2.8)
-----------	-----------------	----------	-------

Inductor:	$v(t) = L \frac{di}{dt}$	$V = j\omega LI$	(2.9)
-----------	--------------------------	------------------	-------

Capacitor:	$i(t) = C \frac{dv}{dt}$	$I = j\omega CV$	(2.10)
------------	--------------------------	------------------	--------

VCVS:	$v_3(t) = \mu v_1(t)$	$V_3 = \mu V_1$	(2.11a)
-------	-----------------------	-----------------	---------

VCCS:	$i_4(t) = g_m v_5(t)$	$I_4 = g_m V_5$	(2.11b)
-------	-----------------------	-----------------	---------


CCVS:	$v_6(t) = r_m i_5(t)$	$V_6 = r_m I_5$	(2.11c)
-------	-----------------------	-----------------	---------

CCCS:	$i_8(t) = \alpha i_7(t)$	$I_8 = \alpha I_7$	(2.11d)
-------	--------------------------	--------------------	---------


Gyrator:	$i_9(t) = G v_{10}(t)$ $i_{10}(t) = -G v_9(t)$	$I_9 = GV_{10}$ $I_{10} = -GV_9$	(2.11e)
----------	---	-------------------------------------	---------

Ideal transformer	$v_1(t) = \frac{1}{n} v_2(t)$	$V_1 = \frac{1}{n} V_2$	(2.12)
	$i_1(t) = -n i_2(t)$	$I_1 = -n I_2$	


نمایش گرافیکی فازور

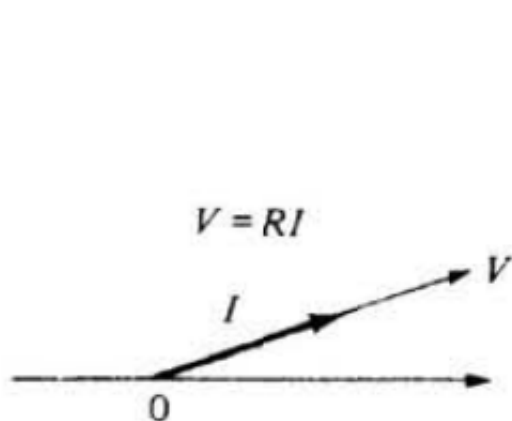

مقاومت

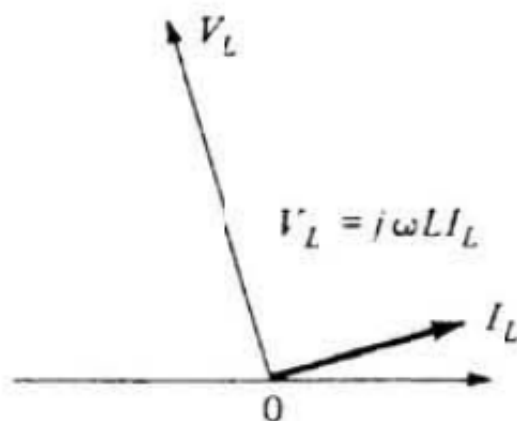


سلف

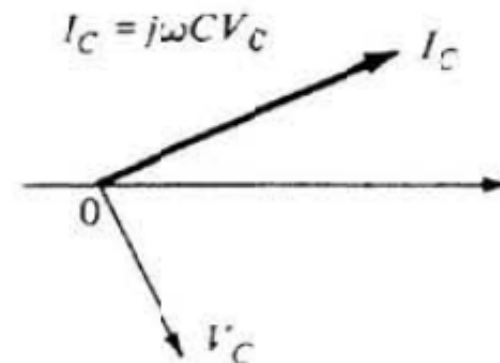

خازن

نمونه مسئله تلگان در حالت دائم سینوسی

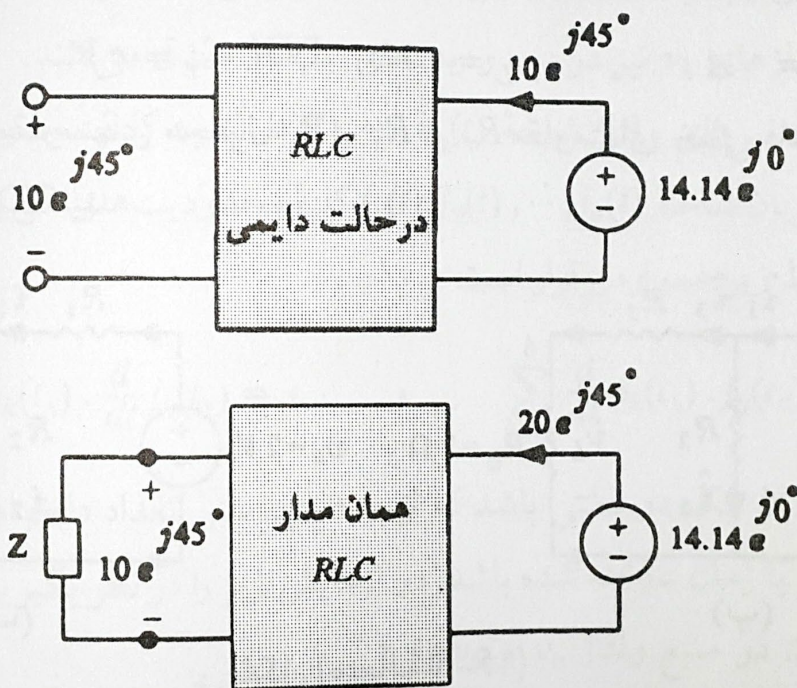۱۹- دو آزمایش در مورد یک مدار RLC در حالت دایمی مطابق شکل (مسأله ۹-۱۹) انجام شد. است. $Z(j\omega)$ را در فرکانس آزمایش به دست آورید.



حل نمونه مسئله



$$10 < 45 * (10 < 45 / Z) + 14.14 < 0 * (-20 < 45)$$

=

$$10 < 45 * 0 + 14.14 < 0 * (-10 < 45)$$

$$(10 < 45 / Z) - 14.14 < 0 = 0$$

$$(10 < 45 / 14.14) = Z = 0.707 < 45$$


نمونه ۲



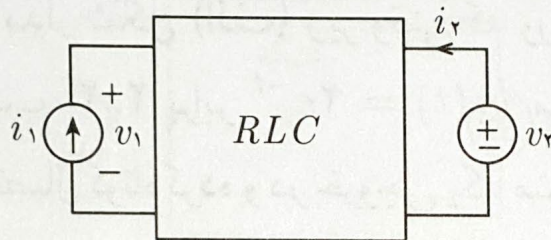۶. در دوقطبی خطی تغییرناپذیر با زمان RLC شکل مقابل اندازه‌گیری‌های زیر در حالت دائمی سینوسی انجام شده است.

«۱۳۷۹»

$v_1(t) = 4\sin(\omega t + 45^\circ)$, $i_2(t) = \sin(\omega t + 60^\circ)$, $v_2 = 0$, $i_1(t) = 2\sin(\omega t + 30^\circ)$
 برای $v_1(t)$, $v_2(t) = \sin \omega t$ و $i_1(t) = \frac{1}{2}\sin(\omega t + 15^\circ)$ کدام است؟



$\sin(\omega t - 60^\circ)$ (۲)

$\frac{1}{2}\sin(\omega t + 30^\circ)$ (۳)

$4\sin(\omega t - 15^\circ)$ (۴)

حل نمونه ۲



شرایط 1	$V_1 = 4 \angle -45^\circ$	$I_1 = 2 \angle -60^\circ$	$V_2 = 0$	$I_2 = 1 \angle -30^\circ$
شرایط 2	$V_1' = ?$	$I_1' = 0.5 \angle -75^\circ$	$V_2' = 1 \angle -90^\circ$	$I_2' = ?$

$$2 \angle -120^\circ = 1 \angle -120^\circ + V_1' * 2 \angle -60^\circ$$

$$V_1' = 0.5 \angle -60^\circ$$



حل دیگری برای نمونه ۲


شرایط 1	$V_1=4<45$	$I_1=2<30$	$V_2=0$	$I_2=1<60$
شرایط 2	$V_1'=?$	$I_1'=0.5<15$	$V_2'=1<0$	$I_2'=?$

$$2<60=1<60+V_1' \cdot 2<30$$

$$V_1'=0.5<30$$


نمونه ۳

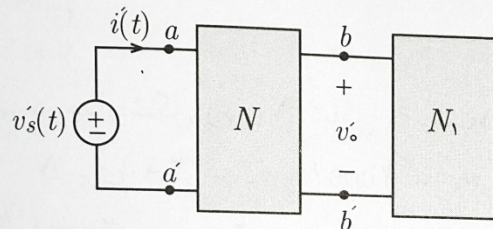۸. دوقطبی N و یک قطبی N_1 فقط از اجزاء R ، L و C خطی تغییرناپذیر با زمان تشکیل شده است. در شکل‌های (الف) و (ب) نتایج دو آزمایش در حالت دائمی سینوسی داده شده است. با توجه به نتایج دو آزمایش، کدامیک از گزینه‌های زیر می‌تواند معادل یک قطبی N_1 باشد؟ «۱۳۷۴»




(ب)
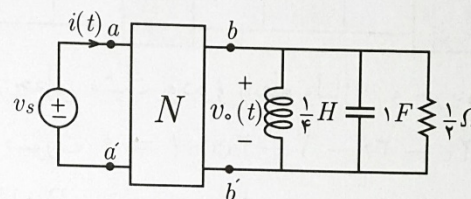
$$\begin{aligned} v_s'(t) &= \sqrt{2} \cos 2t \\ i'(t) &= \cos 2t \\ v_o'(t) &= \cos(2t - 40^\circ) \end{aligned}$$




(الف)

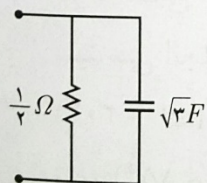
$$\begin{aligned} v_s(t) &= \sqrt{2} \cos 2t \\ i(t) &= \frac{1}{\sqrt{2}} \cos(2t - 60^\circ) \\ v_o(t) &= \frac{1}{\sqrt{2}} \cos(2t - 20^\circ) \end{aligned}$$




(۴)

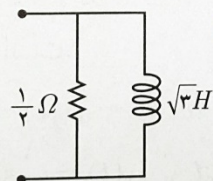

(۳)

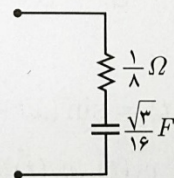

(۲)

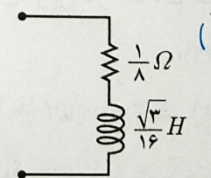

(۱)

حل نمونه ۳



شرایط 1	$V_s = 2 < 0$	$I_s = .5 < -60$	$V_o = .5 < -20$	$I_o = -1 < -20$
شرایط 2	$V_s' = 2 < 0$	$I_s' = 1 < 0$	$V_o' = 1 < -40$	$I_o' = ?$

$$2 < 0 + I_o' \cdot .5 < -20 = 1 < -60 - 1 < -60$$

$$I_o' = -4 < 20$$

ادامه حل نمونه ۳



$$I_o' = -4 \angle 20^\circ$$

$$V_o' = 1 \angle -40^\circ$$

$$Z = \frac{V_o'}{-I_o'} = 0.25 \angle -60^\circ = 0.25 \left(.5 - j \frac{\sqrt{3}}{2} \right) = R + \frac{1}{j\omega C}$$

$$Y = \frac{1}{Z} = 4 \angle 60^\circ = 4 \left(.5 + j \frac{\sqrt{3}}{2} \right) = G + j\omega C$$